
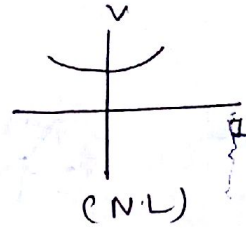
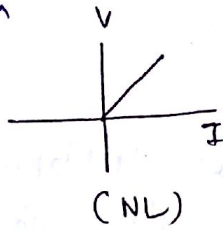




lec-2 → Classification of element

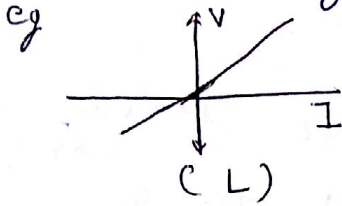- (i) Linear and Non linear element  $\rightarrow$  V-I characteristic show only one eq of straight line passed through origin





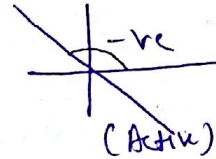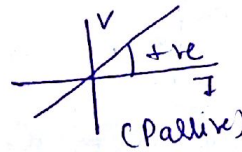- (ii) Active and Passive element  $\rightarrow$  Active - deliver power to ckt  $\rightarrow$  voltage, current, source;  
Passive - otherwise  $\rightarrow$  R, L, C ( $R \geq 0, L, C \geq 0$ )

- ⊙ 1 or 3rd quad  $\rightarrow$  +ve slope  $\rightarrow$  Passive
- ⊙ 2 or 4th quad  $\rightarrow$  -ve slope  $\rightarrow$  Active
- ⊙ 1 or 4th  $\rightarrow$  Active
- ⊙ 2 or 3rd quad  $\rightarrow$  Active




- (11) Unilateral and Bilateral cleft →

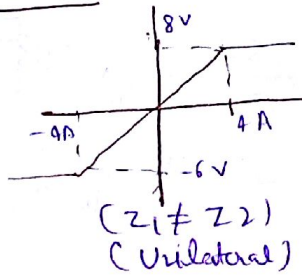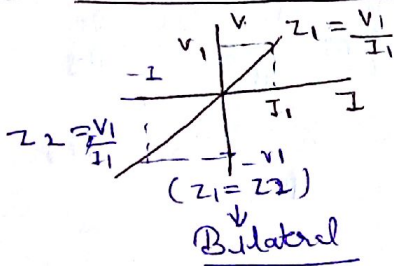

Bilateral - R, L, C      Unilateral → Duct

#  
① linear element  $\Rightarrow$  Bilateral  
Bilateral  $\neq$  linear


- (iv) Time Variant and Time Invariant →

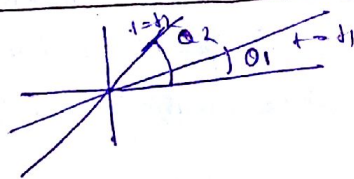


V-I characteristic change w.r to time + the varist  
V-I " remain same - the resist

Lec-2

### Independent Sources

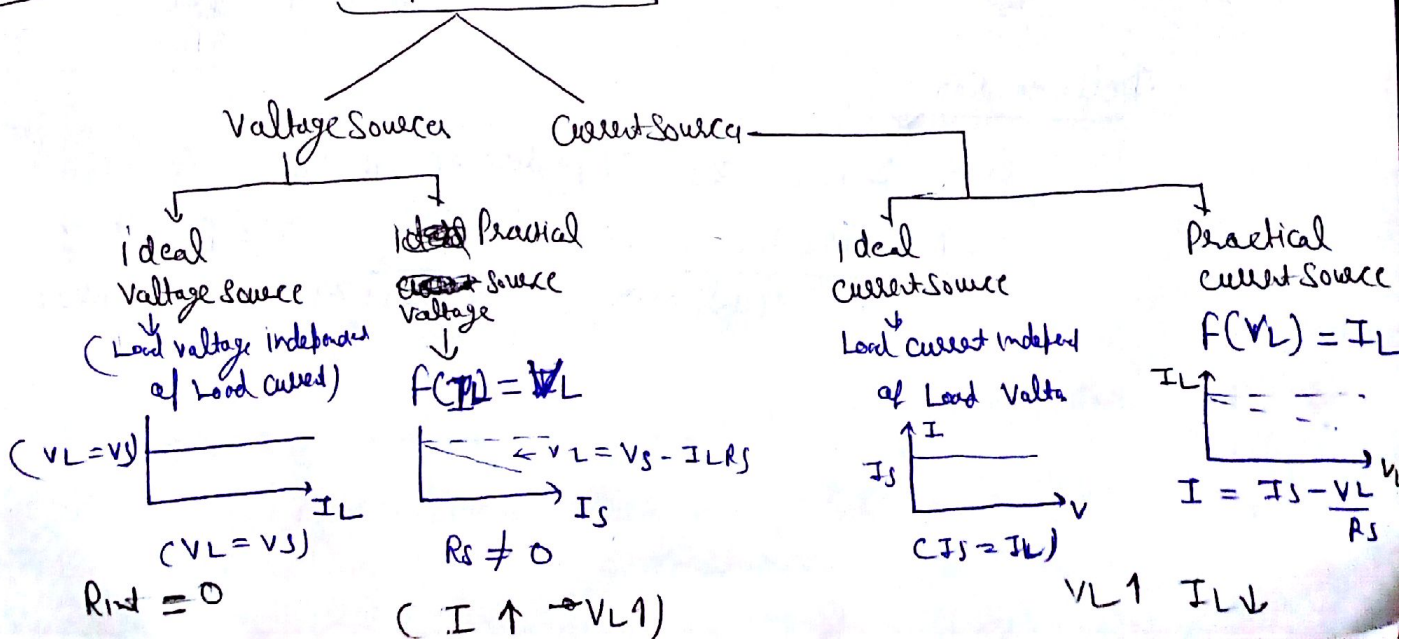


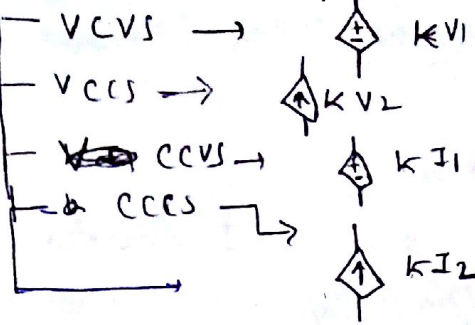(2) Dependent Source

⊙ The Voltage / current of dependent source depends on other circuit parameters.

lec-3

KCL →

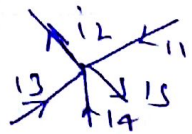


$$i_1 + i_3 + i_4 = i_2 \quad \text{--- Sum of incoming current} \\ = \text{Sum of outgoing current}$$

⊙ follow of Law Conservation of charge

$$\frac{dq_1}{dt} + \frac{dq_3}{dt} + \frac{dq_4}{dt} = \frac{dq_2}{dt}$$



KVL →

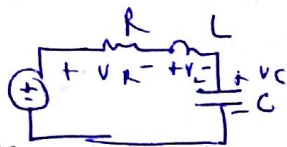



$$V = V_R + V_L + V_C = \frac{d\psi}{dt} = \frac{d\psi_R}{dt} + \frac{d\psi_L}{dt} + \frac{d\psi_C}{dt}$$

⊙ follow of Law of energy Conservation


$$W = W_R + W_L + W_C$$

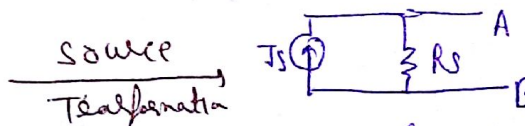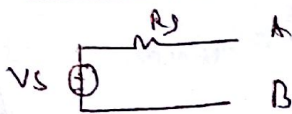Source transformation

$$I_S = \frac{V_S}{R_S}$$

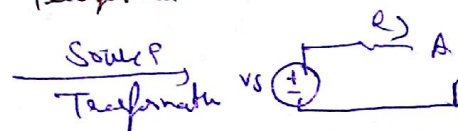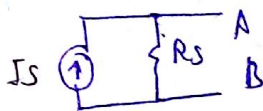

$$V_S = I_S R_S$$

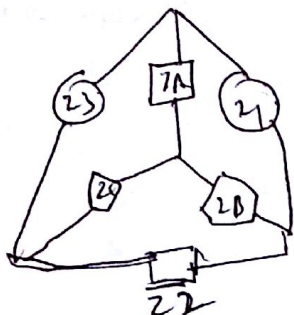Star delta transformation

Star-Delta → Given -  $Z_A, Z_B, Z_C$   
To find -  $Z_1, Z_2, Z_3$

$$Z_1 = (Z_A + Z_B) + \frac{Z_A Z_B}{Z_C}$$

$$Z_2 = (Z_C + Z_B) + \frac{Z_C Z_B}{Z_A}$$

$$Z_3 = (Z_A + Z_C) + \frac{Z_A Z_C}{Z_B}$$

Delta to star

Given  $Z_1, Z_2, Z_3$ , To find  $Z_A, Z_B, Z_C$

$$Z_A = \frac{\text{Product of known}}{\text{Total sum}} = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$


$$Z_B = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3} \quad Z_C = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$



Node Analysis →

$$\begin{array}{c} i_1 \\ \xrightarrow{1} \\ 5V \end{array} \quad 2V \quad \frac{5-2}{1} = +3A \quad \left\{ \frac{4P-LP}{R} \right\}$$
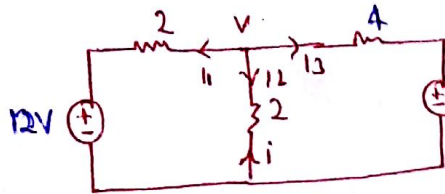
$$\begin{array}{c} -2V \\ \xrightarrow{1} \\ -5V \end{array} = \frac{-2 - (-5V)}{1} = +3A$$




$$\frac{V-12}{2} + \frac{V-0}{2} + \frac{V-5}{4} = 0$$

$$V = 29/5 V, \quad i_2 = \frac{V-0}{2} = 29/10 = 2.9A$$

$$i_1 = +i_2 = -2.9A$$

Mesh Analysis ↓

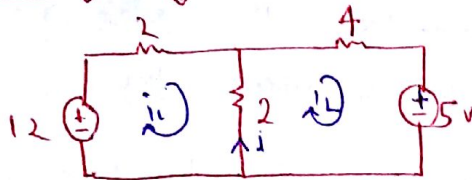

$$2i_1 + 2(i_1 - i_2) = 12$$

$$4i_1 - 2i_2 = 12 \quad \text{--- Mesh 1}$$

$$\text{Mesh}_2 \rightarrow 4i_2 + 5 + 2(i_2 - i_1) = 0$$

$$-2i_1 + 6i_2 = -5 \quad \text{--- (2)}$$


$$i_1 = 3.1 \quad i_2 = 0.2 \quad i_3 = (i_2 - i_1) = -2.9A$$

Tellegen's Theorem ↓

In any N/w the algebraic sum of power at any instant is equal to 0

$$P_{\text{delivered}} = P_{\text{absorbed}}$$

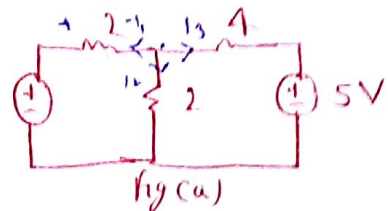- ⊗ - If current enter from +ve and leaves from -ve terminal then that element is absorbing power



- ⊗ - If current enters from -ve and leaves from +ve then element is delivering power




fr fig (a)

$$V = 29/5 V = 5.8V$$


$$i_1 = \frac{12-5.8}{2} = 3.1 \quad i_2 = 2.9A \quad i_3 = 0.2A$$

$$2\Omega, 2\Omega, 4\Omega \text{ \& } 5V - \text{absorbed power} = (P_{2\Omega} + P_{2\Omega} + P_{4\Omega} + P_{5V}) = 37.2 \text{ wJ}$$
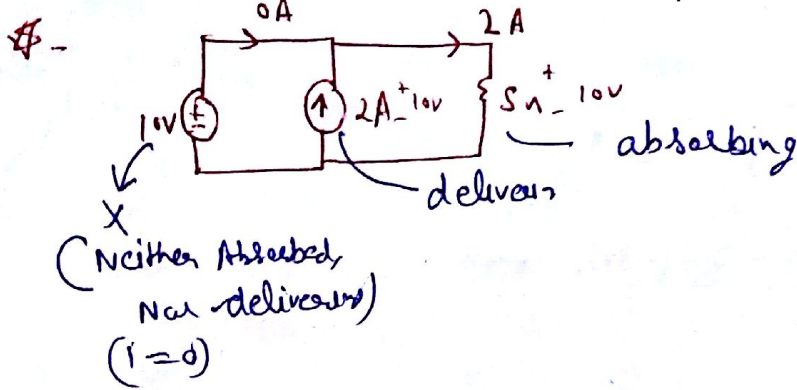
$$12V - \text{delivered power} = P_{12V} = 12 \times 3.1 = 37.2 \text{ wJ}$$




### Lec-6 → N/w Theorem


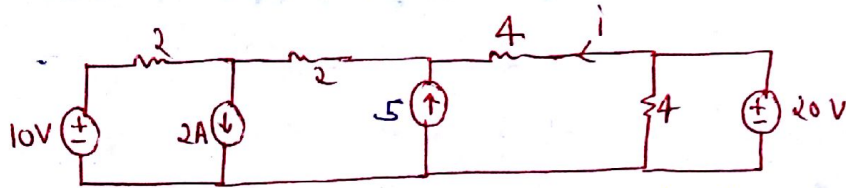


Superposition → Response in a particular branch under algebraic sum of individual Response calculated by treating one independent source at a time

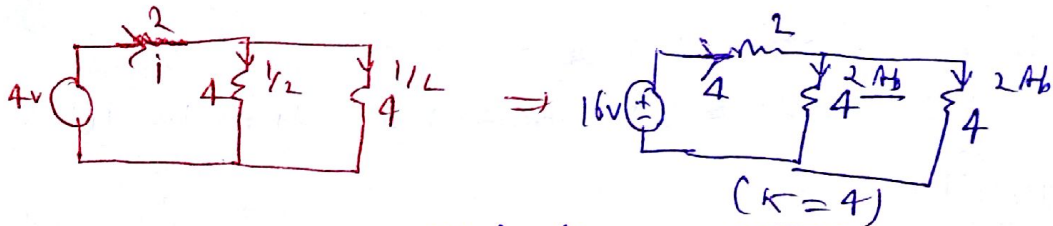Homogeneity - In Linear N/w → excitation  $\times K \Rightarrow$  Response in each branch  $\times K$



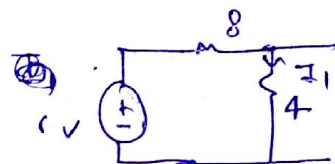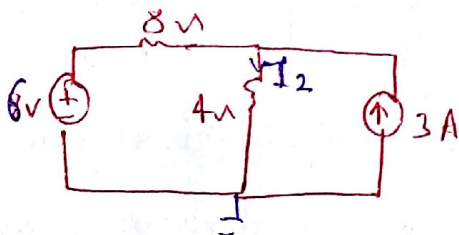- ① Superposition theorem
- Ideal Voltage Source = s.c
  - Ideal current Source = o.c
  - Dependent Source = Leave it





$$I_1 = \frac{6}{12} = 0.5A$$



$$I_2 = 3 \times \frac{8}{12} = 2A$$

$$I = I_1 + I_2 = 0.5 + 2 = 2.5A$$

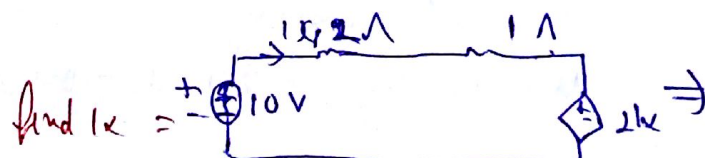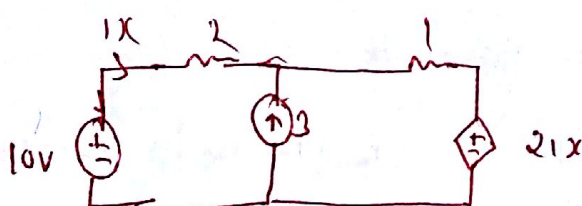

$$I_x = 10 \times \frac{1}{1+2} = 3.33A$$






$$I_x = \frac{3}{2+2} = 0.75A$$

$$I = 3.33 + 0.75 = 4.08A$$



Loc 07

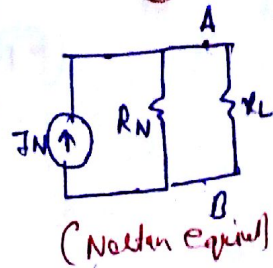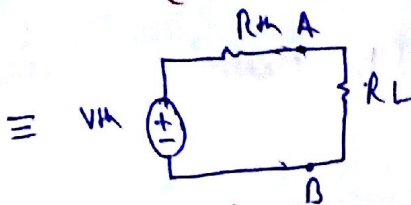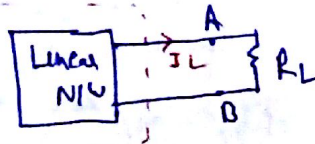Theremin Theorem →  
and  
Norton theorem



$V_{th}$  = O.C Voltage Measured b/w AB by Rem  $R_L$


$$R_{th} = R_{N} = \begin{cases} V.S \rightarrow S.C \\ C.S \rightarrow O.C \end{cases}$$

$$\left\{ \frac{V_{th}}{I_{sc}} \right\}$$


$$I_N \Rightarrow \left\{ \begin{array}{l} S.C \text{ terminal AB find } I_N \\ \left\{ \frac{V_{th}}{R_{th}} \right\} \end{array} \right\} \quad (R_N = R_{th})$$

Method to find Theremin equivalent

Calc-1 - all independent source →

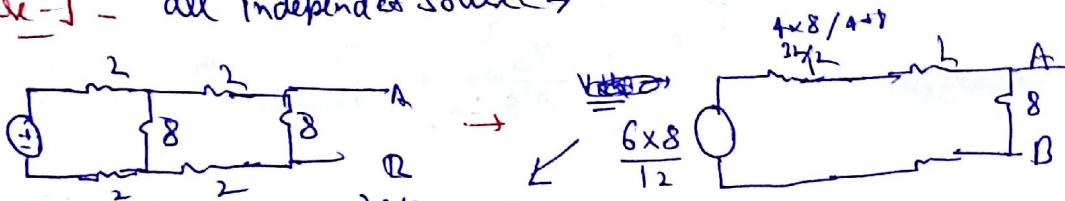

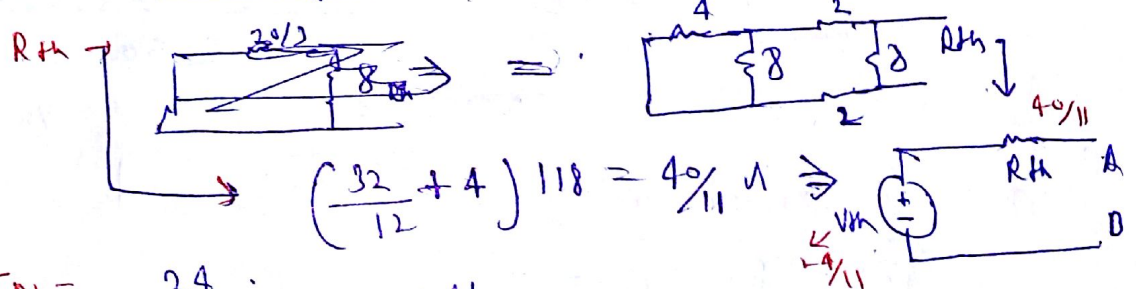
$$4V \text{ source} \rightarrow V_{th} \rightarrow 4 \left( \frac{8}{2 \parallel 8} \right) = 24/11 \text{ volt}$$




$$I_N = \frac{24}{\frac{40}{11}} = 0.6 \text{ A}$$

Calc 3 →

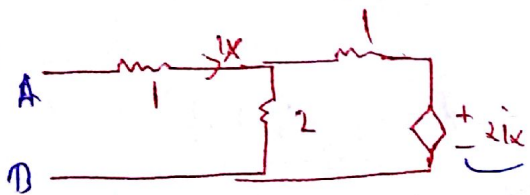

dependent source

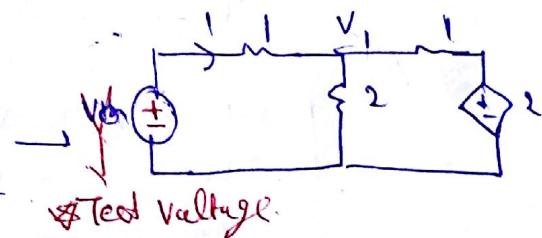

Test Voltage

$$-1 + \frac{V_1}{2} + V_1 - 2i = 0$$

$$\frac{V_1}{2} = i$$

$$i = \frac{V - V_1}{1} \rightarrow V_1 = V - i$$

$$\frac{V - i}{2} = i$$

$$\frac{V}{2} = \frac{3i}{2}$$

$$V/i = 3 = R_{th}$$

Lec 8

(MPTT) - Maximum Power Transfer Theorem →

- ⊙ when Load is Variable
- ⊙ choose Min, internal impedance - otherwise
- ⊙ for Linear, Active, Passive, N/A

Applicable

Circuit 1



( $R_S$  - fixed)  
( $R_L$  - variable)

$$I = \frac{V_S}{R_S + R_L}$$

$$P = I^2 R_L \Rightarrow \frac{V_S^2}{(R_S + R_L)^2} \times R_L$$


$$\frac{dP}{dR_L} = 0 \rightarrow$$

$R_L = R_S \rightarrow$  Maximum Power  
xfer to Load

$$P_L = \frac{V_S^2}{4R_L}$$

$$\eta \approx 50\%$$

Circuit 2 →

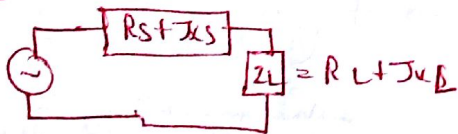

(2(a)) →  $R_L \rightarrow$  variable  $X_L \rightarrow$  fixed

$$R_L = \sqrt{R_S^2 + (X_S + X_L)^2}$$

$\therefore \eta < 50\%$


2(b) -  $R_L$  - fixed  $X_L$  - variable

$$X_L = -X_S$$

2(c) -  $R_L, X_L \rightarrow$  Variable

$$Z_L = R_S - jX_S = Z_S^*$$

Circuit 3 →

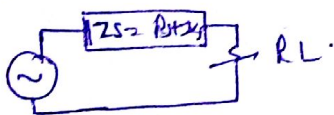

$$R_L = \sqrt{R_S^2 + (X_S)^2}$$

##

If only  $R_L$  is variable →  $R_L = |Z_S|$




If  $X_L$  is variable only -  $X_L = -X_S$

If  $R_L$  and  $X_L$  both variable  $\left. \begin{array}{l} R_L = R_S \\ X_L = -X_S \end{array} \right\} Z_L = Z_S^*$



Lec-9-

(4)

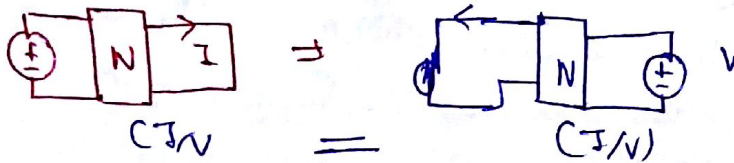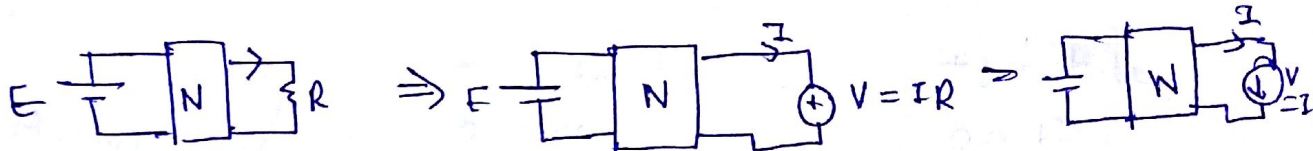
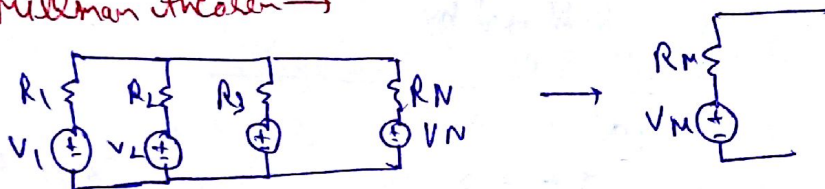
Reciprocity Theorem $(C, L, P, B) \rightarrow$  Response to excitation Active  $\rightarrow$  Constant  $\rightarrow$  I/P and O/P terminals interchanged)Substitution TheoremMillman Theorem

$$V_M = \frac{V_1 G_1 \pm V_2 G_2 \pm V_3 G_3 \pm \dots \pm V_N G_N}{G_1 + G_2 + G_3 + \dots + G_N}$$

$$R_M = \frac{1}{G_1 + G_2 + G_3 + \dots + G_N}$$

\* - Check the polarity of voltage source while adding

Lec-11

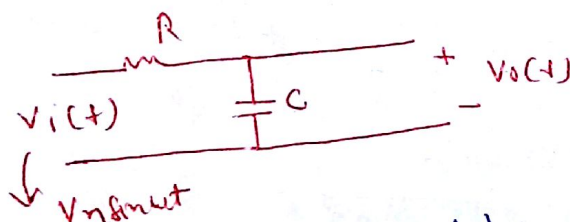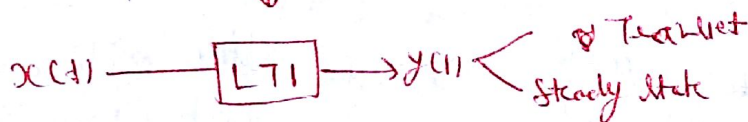Steady State Response

$$v_i(t) = A_i \sin(\omega t + \phi_i) \rightarrow H(s) \rightarrow v_o(t) = A_o \sin(\omega t + \phi_i + \phi_o)$$

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

$$A_o = |H(j\omega)| \text{ at } \omega = \omega_o$$

$$\phi_o = \angle H(j\omega) \text{ at } \omega = \omega_o$$

$$V_o(s) = H(s) * V_i(s)$$

Lec-12

$$\begin{array}{lcl}
 i(t) = I_0 (1 - e^{-t/\tau}) & \rightarrow & \text{charging of inductor} \\
 i(t) = I_0 e^{-t/\tau} & \rightarrow & \text{Discharging of inductor} \\
 v_c(t) = V_0 (1 - e^{-t/\tau}) & \rightarrow & \text{charging of capacitor} \\
 v_c(t) = V_0 e^{-t/\tau} & \rightarrow & \text{Discharging of capacitor}
 \end{array}$$

Behaviour of L, C elements at  $t = 0^+$  and  $t = \infty$

at  $t = 0^+$

$$I_L = 0$$

Inductor Can be Replaced  
By open ckt

at  $t = \infty$

$$V_L = 0$$

Induct Can be  
Replaced by  
S-C

Inductor

at  $t = 0^+$

$$V_C = 0$$

Capacitor act as S-C

at  $t = \infty$

$$I_C = 0$$

Capacitor act as  
open ckt

Capacitor

at  $t = 0^-$  and  $t = 0^+$

$$I_L(0^-) = I_L(0^+)$$

at  $t = 0^-$  and  $t = 0^+$

$$V_C(0^-) = V_C(0^+)$$

Practical value

for  $t \geq 0$

Inductor  $\rightarrow$  Inductor parallel  
with current source

for  $t \geq 0$

Capacitor  $\rightarrow$  Capacitor in series with  
voltage source

Lec-13DC Transient

Source free ckt

- RL ckt
- RC ckt
- RLC ckt

with source  
initial  $t = 0^+$   
and final  $t = \infty$

with source Response  
for  $0 \leq t \leq \infty$  condition



DC transfer (Source free RL N/w) ↓

(1) at  $t = 0^-$

N/w - Steady state - (Inductor - S.C)

(2) at  $t = 0^+$  → Source disconnected

Inductor <sup>Replace</sup> Current source ( $I_L(0^-) = I_L(0^+)$ )

(3) At  $t \geq 0$

$$i_L(t) = I_0 e^{-t/\tau}$$

$$\tau = \frac{L_{eq}}{R_{th}}$$



- equivalent circuit

(14) DC transfer (Source free RC circuit) ↓


(1) - at  $t = 0^-$  → N/w - Steady state → (Capacitor - O.C)

(2) at  $t = 0^+$  → Source disconnected

Capacitor <sup>Replace</sup> voltage source ( $V_C(0^+) = V_C(0^-)$ )

$$v_C(t) = V_0 e^{-t/\tau} \quad \tau = RC$$

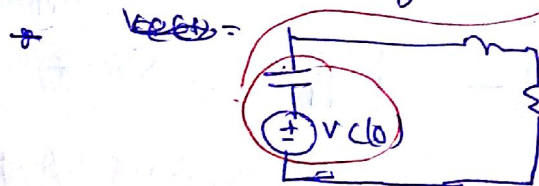Replace Capacitor by → equivalent circuit for  $V_C(t)$ .



(15) - With Source ↓

Initial  $t = 0^+$  and final  $t = \infty$

- Steady state  $\begin{cases} \text{Inductor - S.C} \\ \text{Capacitor - O.C} \end{cases}$
- $I_L(0^-) = I_L(0^+) = 0$  (Inductor - O.C)
- $I_L(0^-) = I_L(0^+) \neq 0$  (Inductor → Current source)
- $V_C(0^-) = V_C(0^+) = 0$  (Capacitor - S.C)
- $V_C(0^-) = V_C(0^+) \neq 0$  (Capacitor - Voltage source)

(3) With source Responced for  $0 \leq t < \infty$  Condition  $\rightarrow$

①  $\rightarrow$  If N/w contain several source, several resistor, several inductor then 
$$I_L(t) = I_L(\infty) + [I_L(0) - I_L(\infty)] e^{-t/\tau} \quad 0 \leq t < \infty$$


②  $\rightarrow$  If above case - if ~~cap~~ Inductor, is replaced by capacitor 
$$V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)] e^{-t/\tau} \quad 0 \leq t < \infty$$

③  $RL, RC$  - not separable  $\rightarrow$  Laplace transform approach needed

LEC-17  $\rightarrow$

AC transient  $\downarrow$

RL ckt

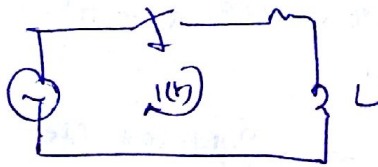

$$i(t) = K e^{-t/\tau} + I_{sc}(t)$$

Phasor  
Approach

Laplace approach

$$v(t) = V_m \sin(\omega t + \phi) \rightarrow \boxed{\frac{1}{R + j\omega L}} \rightarrow V_o(t) = V_m A_0 \sin(\omega t + \phi + \phi_0)$$

$$i(t) = K e^{-t/\tau} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R}\right)$$

$$\boxed{\phi = \tan^{-1} \frac{\omega L}{R}} \rightarrow \text{Transient free state}$$

$$\text{at } t = t_0 \quad \boxed{(\omega t_0 + \phi) = \tan^{-1} \frac{\omega L}{R}} \quad (\text{See function})$$

$$\text{or } (\omega t + \phi) = \tan^{-1} \left( \frac{\omega L}{R} \right) + \frac{\pi}{2} \quad \text{Cosine fun}$$

④ RC ckt

$$v(t) = V_m \sin(\omega t + \phi) \rightarrow \boxed{\frac{1}{1 + j\omega R}} \rightarrow V_o(t) = V_m A_0 \sin(\omega t + \phi + \phi_0)$$

$$\boxed{\phi = \tan^{-1} \omega R C}$$

Transient free RC ckt



$$\boxed{(\omega t + \phi)_{t=t_0} = \tan^{-1} \omega R C}$$

$$\boxed{(\omega t + \phi)_{t=t_0} = \tan^{-1} \omega R C + \pi/2}$$

⑤ RLC ckt  $\rightarrow$   
NO Transient  
Free Condition



Two Port N/W

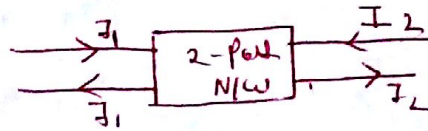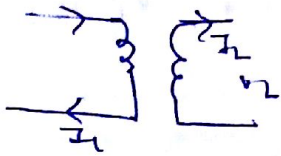

(1) Z-parameter (Z) - (O.C Parameter)

$$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned}$$

$V_1, V_2$  - Dependent  
 $I_1, I_2$  - Independent

Symmetrical  $= Z_{11} = Z_{22}$   
Reciprocal  $= Z_{12} = Z_{21}$

(2) Y parameter (Short ckt Parameter)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Symmetrical:  $Y_{11} = Y_{22}$   
Reciprocal:  $Y_{12} = Y_{21}$

(3) ABCD Parameter (T Parameter)

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Symmetrical  $A = D$   
Reciprocal  $AD - BC = 1$

(4) T' Parameter

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & D' \\ C' & B' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

Symmetrical  $= A' = D'$   
Reciprocal  $= A'D' - B'C' = 1$

(5) h-parameter

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


Symmetrical  $\rightarrow h_{11}h_{22} - h_{12}h_{21} = 1$   
Reciprocal  $= h_{12} = -h_{21}$

(6) g-parameter


$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

Symmetrical  $= g_{11}g_{22} - g_{12}g_{21} = 1$   
Reciprocal  $\rightarrow g_{12} = -g_{21}$

Z parameter of T N/W

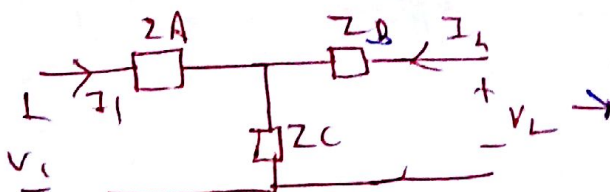


$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} (Z_A + Z_B) & Z_B \\ Z_C & (Z_A + Z_C) \end{bmatrix}$$

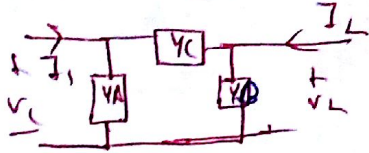Y Parameter of  $\pi$ -N/w

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_A + Y_C & -Y_C \\ -Y_C & Y_C + Y_D \end{bmatrix}$$


T Parameter of Inverted L

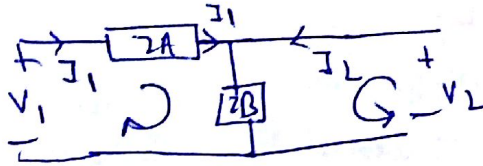

$$\begin{aligned} A &= \frac{Z_A + Z_B}{Z_B} & B &= -Z_A \\ C &= \frac{1}{Z_B} & D &= 1 \end{aligned}$$

(Case-1)

(i) Series Connection

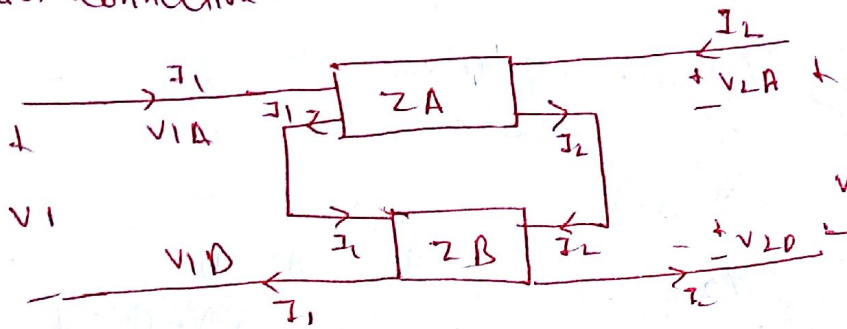

$$\begin{pmatrix} V_{1A} \\ V_{2A} \end{pmatrix} = (Z_A) \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \quad \text{--- (1)}$$

$$V_1 = V_{1A} + V_{1B}$$


$$V_2 = V_{2A} + V_{2B}$$

$$\begin{pmatrix} V_{1B} \\ V_{2B} \end{pmatrix} = (Z_B) \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \quad \text{--- (2)}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = (Z_A + Z_B) \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$


$$Z_{eq} = Z_A + Z_B$$

(ii) Parallel Connection

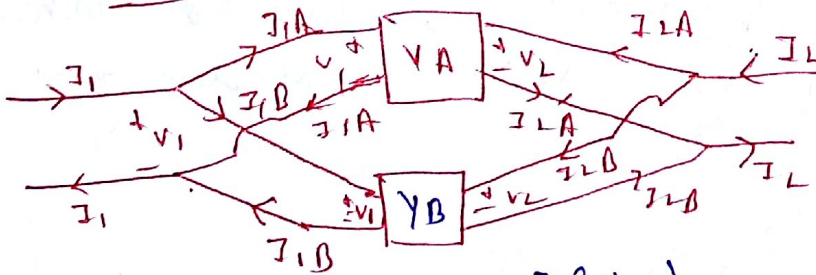

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = [Y_A + Y_B] \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$


(iii) Cascade Connection

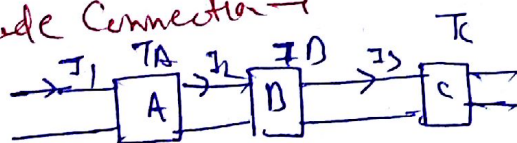

$$T_{tot} = (T_A)(T_B)(T_C)$$




## AC Analysis

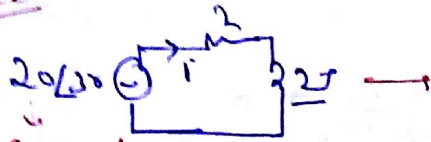

Take RMS value  
When nothing is  
mentioned

$$I = \frac{20\angle 30}{2\angle 0} = \frac{10}{2}\angle -15 = 5\angle -15 \text{ (RMS value)}$$
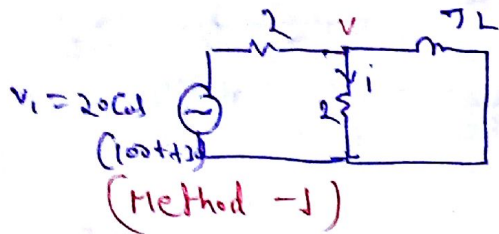
$$I_{\max} = \sqrt{2} I_{\text{RMS}} = \sqrt{2} \times 5\angle -15 = 7.07\angle -15$$




$$V_i = 20\cos(100t + 30)$$

$$\frac{V - 20\angle 30}{2} + \frac{V}{2} + \frac{V}{2j} = 0$$

$$V = 4\angle 56.56$$

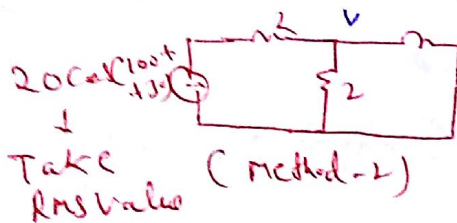or  $I_1 = \frac{V}{2} = 2\sqrt{5}\angle 56.56 = 2\sqrt{5}\cos(100t + 56.56)$



Take RMS value (Method -2)

$$\frac{V - \frac{20}{\sqrt{2}}\angle 30}{2} + \frac{V}{2} + \frac{V}{2j} = 0$$

$$V = 2\sqrt{10}\angle 56.56 \quad i_{\text{RMS}} = \frac{V}{2} = \sqrt{10}\angle 56.56$$

$$I_{\max} = i_{\text{RMS}} \times \sqrt{2} = \sqrt{20}\angle 56.56 = 4.47\angle 56.56$$


$(a+bi) \rightarrow A\angle\theta \rightarrow A = \sqrt{a^2+b^2} \quad \theta = \tan^{-1} b/a$   
 $A\angle\theta \rightarrow (a+bi) \rightarrow a = A\cos\theta \quad b = A\sin\theta$   
 (Polar-Rectangular Conversion)


### Bullated point

- when nothing is given about excitation then always taken that value as RMS value
- ① when <sup>only</sup> sinusoidal excitation is given then taken sine as Ref.
- ② when only cosinusoidal " " " " " " Cos as Ref.
- ③ when both sine, cosine excitation have same freq is given then taken anyone as Ref. and make other as same Ref.
- ④ when both sine and cosine excitation have diff. freq is given then only superposition theorem can be applicable.


LEC-21 -

Series RL Circ -

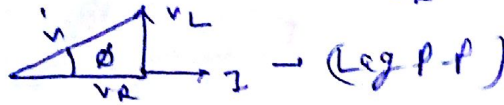

 $\rightarrow V_R = IR, V_L = I\omega L \quad \tan \phi = \frac{V_L}{V_R} \Rightarrow \phi = \tan^{-1} \frac{V_L}{V_R} = \tan^{-1} \frac{\omega L}{R}$



Series RC Circ

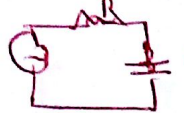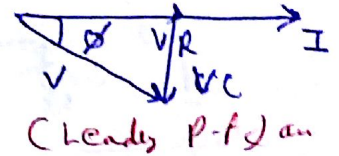
 $\rightarrow V_R = IR, V_C = \frac{I}{\omega C} = \left| \frac{I\phi}{\omega C} \right| \angle -90^\circ$ 

$$\phi = \tan^{-1} \frac{V_C}{V_R} = \tan^{-1} \frac{1}{\omega RC}$$



Series RLC Circ



$V_L > V_C \rightarrow \text{Lag} \rightarrow \tan^{-1} \left( \frac{\omega L - \omega C}{R} \right) - \text{p.f.}$

$V_C > V_L - \text{Lead} - \tan^{-1} \left( \frac{\omega C - \omega L}{R} \right) - \text{p.f.}$

$V_L = V_C \rightarrow \phi = 0 - \text{ (Resonance Condition) } (\omega L = \omega C)$

Parallel RLC Circ

$\cos \phi = \frac{I_R}{I} \quad \phi = \tan^{-1} \left( \frac{I_L}{I_R} \right) - (\text{Lag})$

Parallel RC Circ  $\rightarrow \phi = \tan^{-1} \left( \frac{I_C}{I_R} \right) \rightarrow \text{Leading p.f.}$

Parallel RLC Circ  $\rightarrow I_L = \left| \frac{V}{\omega L} \right| \angle 90^\circ \quad I_C = \left| \frac{V}{\omega C} \right| \angle -90^\circ \rightarrow \left( \frac{I_C - I_L}{I_R} \right)$

$$\phi = \tan^{-1} \left( \frac{I_C - I_L}{I_R} \right) \quad \text{or } \phi = \tan^{-1} \left( \frac{I_C - I_L}{I_R} \right)$$

(Lead) Lag Resonance

Power  $\rightarrow$

$P_{(+) = V_m I_m \cos(\theta_v - \theta_i)$

$S = V_m I_m^*$

$P_{avg} = V_m I_m \cos(\theta_v - \theta_i) - \text{Active Power}$


$Q_{avg} = V_m I_m \sin(\theta_v - \theta_i) - \text{Reactive Power}$

R Load  $\rightarrow \theta_v = \theta_i \quad Q = 0$

L Load  $\rightarrow \theta_i = -90^\circ \quad Q = V_m I_m > 0$

C Load  $\rightarrow \theta_i = +90^\circ \quad Q = -V_m I_m < 0$

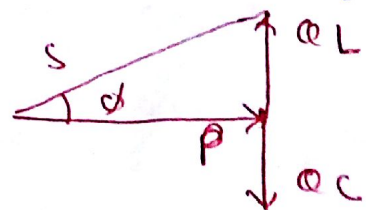$\cos \phi = \frac{\text{Useful Power}}{\text{net power}} =$





## Resonance

Quality factor  $Q = \frac{2\pi \times \text{Max energy store}}{\text{energy dissipated in 1 cycle}} = \frac{\text{Reactive Power}}{\text{Active Power}}$

$\text{---} \frac{R}{L} \text{---} \Rightarrow Q = \frac{XL}{R} = \frac{\omega L}{R}$

Dissipation factor  $D = \frac{1}{Q}$

S.No	Type	Quality factor
1	$\text{---} \frac{R}{L} \text{---}$	$Q = 0$
2	$\text{---} \frac{L}{C} \text{---}$	$Q = \infty$
3	$\text{---} \frac{C}{L} \text{---}$	$Q = \infty$
4	$\text{---} \frac{L}{R} \text{---}$	$Q = \omega L / R$
5	$\text{---} \frac{R}{C} \text{---}$	$Q = \frac{1}{\omega CR}$
5	$\text{---} \frac{L}{R} \text{---}$	$Q = \frac{\omega L}{R} = \frac{1}{\omega CR} = \frac{1}{R} \sqrt{L/C}$
6	$\text{---} \frac{R}{L} \text{---}$	$Q = R / XL = R / \omega L$
7	$\text{---} \frac{C}{L} \text{---}$	$Q = \omega CR$
8	$\text{---} \frac{L}{C} \text{---}$	$Q = R \sqrt{C/L}$

## Series Resonance $\rightarrow$



$f_0 = \frac{1}{2\pi\sqrt{LC}}$

$I = \text{Max} = \frac{V}{Z} = \frac{V}{R}$

$V_R = V$

$V_L = jQV$

$V_C = -jQV$

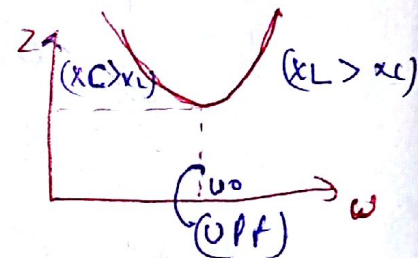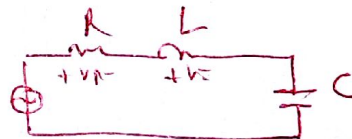

(Bandwidth)  $\rightarrow$   $BW \downarrow$  no of channel  $\uparrow$   
 $P \geq \frac{1}{2} P_{\text{max}} \rightarrow \text{good effect}$   
 $(BW = \omega_2 - \omega_1)$


Cut off freq

$\omega_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$

$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$


$BW = R/L$

$f_2 - f_1 = R / (2\pi L)$

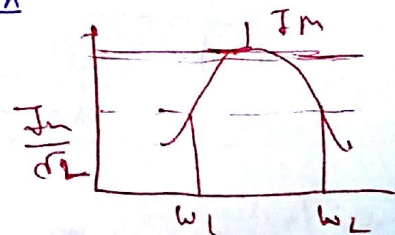


$Q = \frac{\omega_0}{BW}$

True Cost

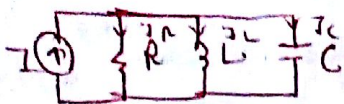Parallel Resonance

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

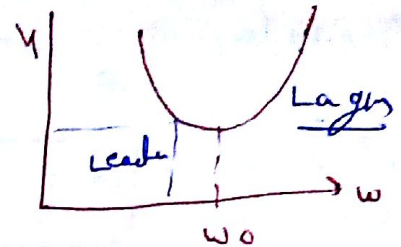

$Q\omega \Rightarrow f \geq 2 \text{ P.M.H.} - \text{good steel}$   
find out off  $f_{res}$

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(-\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$BW = \omega_2 - \omega_1 = \frac{1}{RC} = \frac{\omega_0}{Q} = \frac{1}{\text{the Q factor}}$$

Lec-25

Magnetically coupled circuit  $\rightarrow$

Calc-1

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Calc-2

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Coupling Coefficient  $\rightarrow$




$$E = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

$K=0 - M=0 \rightarrow$  Isolated coil


$K=1 - K=\sqrt{L_1 L_2} -$  Tightly coupled

Series Aiding  $\rightarrow$

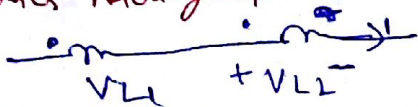


$$L_{eq} = L_1 + L_2 + 2M$$

Series opposing

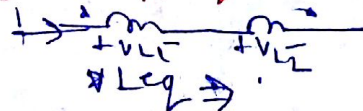

$$L_{eq} = L_1 + L_2 - 2M$$

Parallel aiding

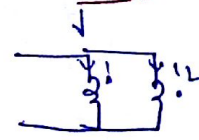

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

Parallel opposing



$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$