

(2)

Code : 031609

B.Tech 6th Semester Exam., 2016

POWER ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Choose the correct option (any seven) : $2 \times 7 = 14$

(a) A single-phase one pulse diode rectifier is feeding an RL load with freewheeling diode across the load. For conduction angle β , the main diode and freewheeling diode would, respectively, conduct for

- (i) $\pi, \pi - \beta$
- ~~(ii) $\pi, \beta - \pi$~~
- (iii) β, π
- (iv) $\beta - \pi, \pi$

(b) When a thyristor is forward biased, the number of blocked p-n junctions is

- ~~(i) 1~~
- (ii) 2
- (iii) 3
- (iv) 4

(c) During forward blocking state, a thyristor is associated with

- ~~(i) large current, low voltage~~
- ~~(ii) low current, large voltage~~
- (iii) medium current, large voltage
- (iv) low current, medium voltage

(d) When a UJT is used for triggering an SCR, the wave shape of the voltage obtained from UJT circuit is a

- (i) sine wave
- ~~(ii) sawtooth wave~~
- (iii) trapezoidal wave
- (iv) square wave

(e) In a commutation circuit employed to turn off an SCR, satisfactory turn-off is obtained when

- (i) circuit turn-off time < device turn-off time
- ~~(ii) circuit turn-off time > device turn-off time~~
- (iii) circuit time constant > device turn-off time
- (iv) circuit time constant < device turn-off time

AK16/677

(Turn Over)

AK16/677

(Continued)

(3)

- (f) A step-up chopper has V_s as the source voltage and α as the duty cycle. The output voltage for this chopper is given by
- (i) $V_s(1+\alpha)$
 - ~~(ii) $V_s/(1-\alpha)$~~
 - (iii) $V_s(1-\alpha)$
 - (iv) $V_s/(1+\alpha)$
- (g) In an inverter with fundamental output frequency of 50 Hz, if third harmonic is eliminated, then the frequencies of other components in the output voltage wave, in Hz, would be
- (i) 250, 350, 450, high frequencies
 - (ii) 50, 250, 350, 450
 - ~~(iii) 50, 250, 350, 550~~
 - (iv) 50, 100, 200, 250
- (h) A cycloconverter is a frequency converter from
1. higher to lower frequency with one-stage conversion
 2. higher to lower frequency with two-stage conversion
 3. lower to higher frequency with one-stage conversion
 4. AC at one frequency to DC and then DC to AC at different frequencies

AK16/677

(Turn Over)

(4)

From these, the correct statement(s) is/are

- (i) 2, 4
 - (ii) 1 only
 - (iii) 2, 3
 - (iv) 1, 3
- (i) If, for a single-phase half-bridge inverter, the amplitude of output voltage is V_s and the output power is P , then their corresponding values for a single-phase full-bridge inverter are
- (i) V_s, P
 - (ii) $2V_s, P$
 - (iii) $2V_s, 2P$
 - ~~(iv) $2V_s, 4P$~~
- (j) In DC choppers, the waveforms for input and output voltages are respectively
- (i) discontinuous, continuous
 - ~~(ii) both continuous~~
 - (iii) both discontinuous
 - (iv) continuous, discontinuous
2. (a) Briefly discuss the V-I characteristic of SCR. 6
- (b) Explain the turn-on and turn-off characteristics of SCR with neat waveforms. 8

AK16/677

(Continued)

3. (a) Explain the operation of three-phase half-wave controlled converter for a firing angle less than 30° and feeding R load. Also derive the expression for its average output voltage. 8

(b) The specification sheet for an SCR gives maximum rms on-state current as 35 A. If this SCR is used in a resistive circuit, compute average on-state current rating for half sine wave current for conduction angle of 180° . 6

4. (a) Explain the effect of source inductance in the operation of single-phase fully controlled converter. 8

(b) With neat circuit diagram and waveform, explain the working principle of single-phase AC voltage controller with R - L load. 6

5. (a) Explain the principle of operation of three-phase inverter with 180° conduction mode with necessary waveforms and circuit. 8

(b) A step-up chopper has input voltage of 220 V and output voltage of 660 V. If the conducting time of thyristor-chopper is $100\mu\text{s}$, compute the pulse width of output voltage. In case output-voltage pulse width is halved for constant frequency operation, find the average value of new output voltage. 6

6. (a) Explain the two-transistor analogy of a thyristor. 7

(b) Discuss the various mechanisms that can be used to trigger thyristors. 7

7. (a) Discuss the operation of step-up chopper and prove that its output voltage is greater than input voltage. 8

(b) Snubber circuit for an SCR should primarily consist of capacitor only. But, in actual practice, a resistor is used in series with capacitor. Discuss. 6

8. (a) With neat circuit diagram and waveform, explain the operating principle of $1-\phi$ to $1-\phi$ step down mid-point type cycloconverter, with continuous load current. Assume the loads to be R and L in series. 8

(7)

(b) A single-phase half-wave AC voltage controller feeds a load of $R = 20 \Omega$ with an input voltage of 230 V, 50 Hz. Firing angle of thyristor is 45° . Determine—

(i) rms value of output voltage;

(ii) average input current. 6

9. Briefly discuss the different types of PWM schemes available for voltage control in an inverter. 14
